

# 문제 풀이(반 MCLC 유사문제).

## 1. MCLC 시스템

1) 외부에서 주어진 입력  $f(t)$ , 출력은 하지 X.

$$m\ddot{x} + f(t) = kx + D\dot{x}$$

$$\zeta^2 m \ddot{x} + f(t) = kx + \zeta D \dot{x}$$

$$\zeta^2 m \ddot{x} - \zeta D \dot{x} - kx = -f(t)$$

$$\zeta^2 \ddot{x} - \zeta \frac{D}{m} \dot{x} - \frac{k}{m} x = -\frac{1}{m} f(t)$$

$$\begin{bmatrix} \ddot{x} \\ \dot{x} \end{bmatrix} = \begin{bmatrix} \frac{D}{m} & \frac{k}{m} \\ 1 & 0 \end{bmatrix} \begin{bmatrix} \dot{x} \\ x \end{bmatrix} + \begin{bmatrix} -\frac{1}{m} \\ 0 \end{bmatrix} f(t)$$

## 2. RLC 시스템

입력:  $E(t)$  출력은  $V_C(t)$

$$E(t) = \zeta L i(t) + \frac{1}{\zeta C} V_C(t) + R i(t)$$

$$E(t) = i(t) \left\{ \zeta L + \frac{1}{\zeta C} + R \right\}$$

$$E(t)$$

Q1) 2, E(t). 2?

$$E(t) = \zeta L i(t) + \frac{1}{C} \gamma(t) + R i(t)$$

$$(E(t)) = (\zeta^2 L i(t) + \frac{1}{C} \gamma(t) + R \zeta \gamma(t))$$

$$i(t) (\zeta^2 L + R \zeta + \frac{1}{C}) = S E(t)$$

$$\frac{i(t)}{E(t)} = \frac{s}{\zeta^2 L + R \zeta + \frac{1}{C}} \quad \text{2nd: } \zeta i(t) = \dot{i}(t)$$

$$\begin{bmatrix} i(t) \\ \dot{i}(t) \end{bmatrix} = \begin{bmatrix} -\frac{R}{\zeta} & -\frac{1}{\zeta C} \\ 1 & 0 \end{bmatrix} \begin{bmatrix} i(0) \\ \dot{i}(0) \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} E(t)$$

$$\zeta^2 \gamma(t) = -\frac{R}{\zeta} S i(0) - \frac{1}{\zeta C} \dot{i}(0)$$

$$y(t) = \zeta i(t) = \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} i(0) \\ \dot{i}(0) \end{bmatrix}$$

$$L \hookrightarrow m \quad D \hookrightarrow R \quad \frac{1}{C} = K.$$